

- Q.6 Majority carriers in N-Type semiconductor is
- a) Holes
 - b) Electrons
 - c) Both
 - d) None

SECTION-B

Note: Objective/Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 What is recombination of electrons and holes?
- Q.8 Define doping?
- Q.9 Define Biasing.
- Q.10 What is rectifier?
- Q.11 What is Class A amplifier?
- Q.12 Define Slew rate.

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Explain working of Zener diode as voltage regulator.
- Q.14 Explain intrinsic semiconductor.
- Q.15 Explain P type semiconductor.
- Q.16 Explain working of transistor as an amplifier.

(2)

220824

- Q.17 Explain voltage divider biasing.
- Q.18 Explain working of half wave rectifier.
- Q.19 Explain working of 7805 voltage regulator.
- Q.20 What is feed back? Write advantages of feed back.
- Q.21 Explain working of Inverting amplifier.
- Q.22 Explain working of 555 timer as astable multivibrator.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Explain VI characteristics of P-N junction diode.
- Q.24 Explain working and frequency response of two stage RC coupled amplifier.
- Q.25 Write short note on (any two)
- a) Mosfet
 - b) RC Phase shift oscillator
 - c) Applications of op-amp

(3)

220824

No. of Printed Pages : 4

220824

Roll No.

2nd Sem / Branch : Computer Engg.
Sub.: Analog Electronics

Time : 3Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 The number of diodes required in centre tap rectifier

- a) 4
- b) 2
- c) 1
- d) None

Q.2 Diode normally works in

- a) Forward Bias
- b) Reverse Bias
- c) Both
- d) None

Q.3 Transistor can work as switch

- a) Yes
- b) No

Q.4 _____ type of feedback is used oscillators.

- a) Negative feedback
- b) Positive feedback

Q.5 FET is essentially a

- a) Current driven device
- b) Voltage driven device
- c) Power driven device
- d) None

(2200)

(4)

220824

(1)

220824