

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

Q.23 Explain transistor as an amplifier in CE configuration, and calculation of current gain and voltage

Q.24 Compare JFET and BJT.

Q.25 Difference between P and N type semiconductors and energy level diagram.

(920)

(4)

221024/212821

No. of Printed Pages : 4

Roll No.

221024/212821

2nd Sem. / ECE, Automation & Robotics

Subject : Electronic Devices and Circuits - I

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 In the depletion region of a pn junction, there is a shortage of _____. (CO2)

- a) Acceptor
- b) Holes and electrons
- c) Donor ions
- d) None

Q.2 At room temperature the intrinsic semiconductor behaves as _____

- a) Copper wire
- b) Insulator
- c) Semiconductor
- d) Conductor

Q.3 The breakdown of PN Junction diode due to high potential gradient is called _____

- a) Voltage breakdown
- b) Zener breakdown
- c) Current breakdown
- d) None

(1)

221024/212821

- Q.4 The common base current gain is _____.
- a) Less than 1 b) Equal to 1
c) Usually 10-15 d) Usually 50-150
- Q.5 For faithful amplification of signals, the transistors must be operated in _____ region
- a) Active b) Saturation
c) Cutoff d) reverse
- Q.6 Ideally an amplifier must have _____ input resistance.
- a) Zero b) Low
c) Medium d) Infinite

SECTION-B

- Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)
- Q.7 N type semiconductor is made by doping _____ impurities.
- Q.8 The small amount of AC present in filters in filters output is called _____
- Q.9 In active region of operation the collector junction is _____ biased.
- Q.10 The ideal value of stability factor is _____

(2) 221024/212821

- Q.11 AC load line and DC load line intersect at _____
- Q.12 FET stands for _____.

SECTION-C

- Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)
- Q.13 Explain Zener breakdown.
- Q.14 Write a note on Shunt capacitor filter and LC filter
- Q.15 Explain VI characteristics of diode.
- Q.16 Explain the mechanism of current flow in PNP transistor.
- Q.17 Explain the operation of FET and its applications
- Q.18 Explain intrinsic and extrinsic semiconductor.
- Q.19 Explain the working of full wave bridge rectifier.
- Q.20 Explain the concept of transistor biasing and operating point.
- Q.21 Explain the concept of transistor biasing and operating point.
- Q.22 Explain the input and output characteristics of CE configuration.

(3) 221024/212821